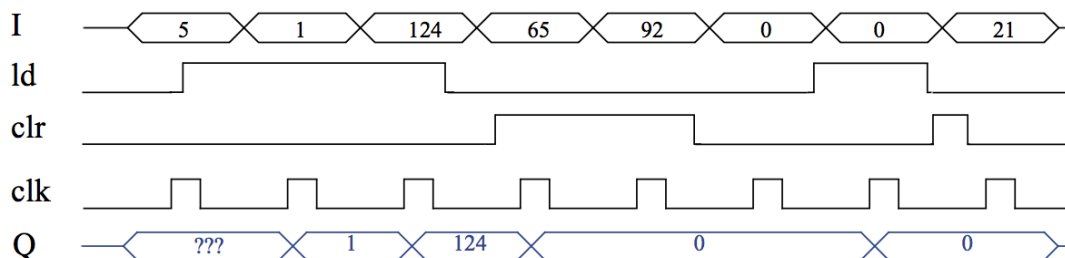



Computer Organization

Homework Set # 2


4.2 Solution: (10', 2.5' each number)



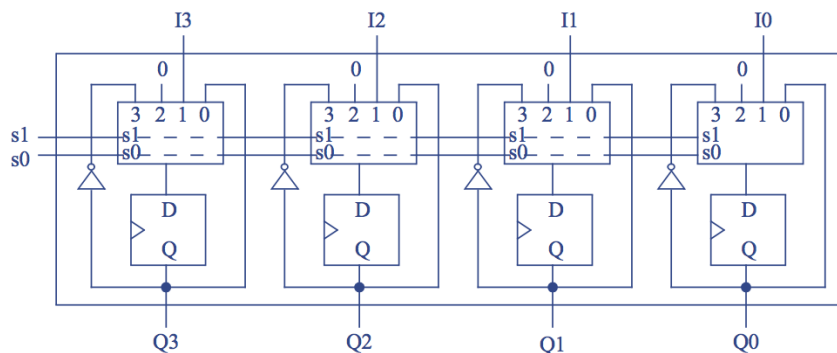4.3 Solution: (10', should be all correct, careless mistakes -2')



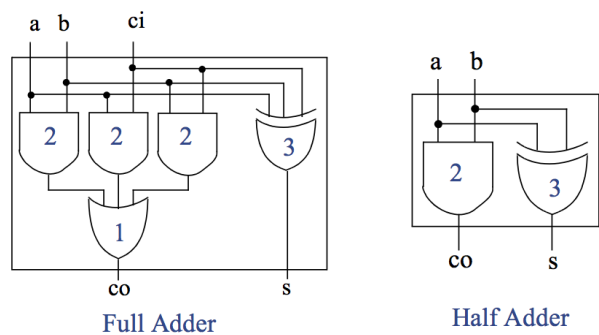4.10 Solution: (10', only shows final answer without workout gets 4')




From the illustration above, we see that both the FA and HA have a maximum gate delay of 3 ns. Therefore, $8 \text{ adders} \times 3 \text{ ns/adder} = 24 \text{ ns}$ is required for an 8-bit carry-ripple adder to ensure a correct sum is on the adder's output.

An answer of 23 ns is also acceptable since the carry out of a half-adder will be correct after 2 ns, not 3 ns, and a half-adder may be used for adding the first pair of bits (least significant bits) if the 8-bit adder has no carry-in.


4.13 Solution: (10', should be all correct, careless mistakes -2')

$$((A+B)+C)+D$$

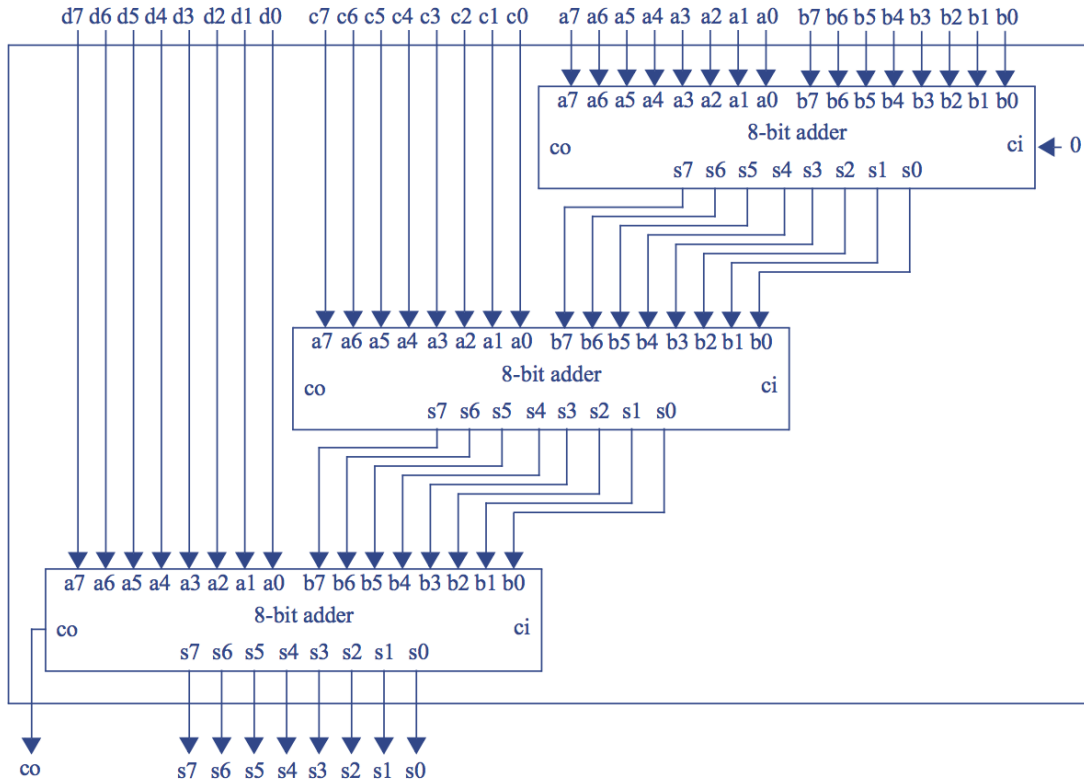

Another correct solution would add C+D, and then add the results to the result of A+B. That solution also uses just three adders, but actually has less delay. $(A+B)+(C+D)$

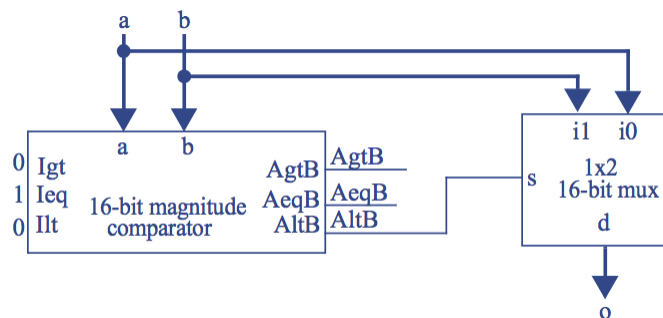4.21 Solution: (10', should be all correct, careless mistakes -2')




4.30 Solution: (5', 1' each)

- a) -32
- b) 127
- c) -16
- d) -64
- e) -32

4.33 Solution: (10' all correct, 0 all wrong, -1' per wrong answer)

- a) 00011101
- b) 01100100
- c) 01111101
- d) 11100011
- e) 10011100
- f) 10000011
- g) 11111110

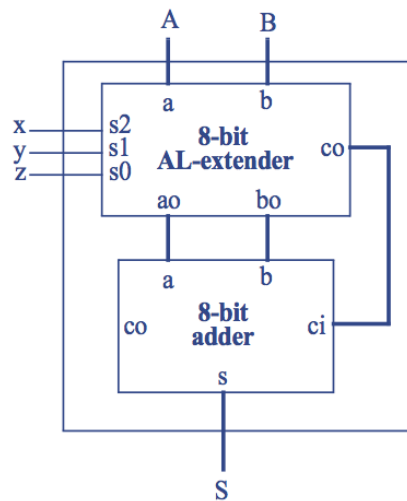4.40 Solution: (10': 2' for design architecture, 1' for each operation)



Operation of the AL-extender:

When xyz=000, ao=a, bo=b', co=1

When xyz=001, ao=a, bo=b, co=0

When xyz=010, ao=a<<3, bo=0, co=0

When xyz=011, ao=a>>3, bo=0, co=0


When xyz=100, ao=a NAND b, bo=0, co=0

When xyz=101, ao=a XOR b, bo=0, co=0

When xyz=111, ao=a reversed, bo=0, co=0

When xyz=111, ao=NOT a, bo=0, co=0

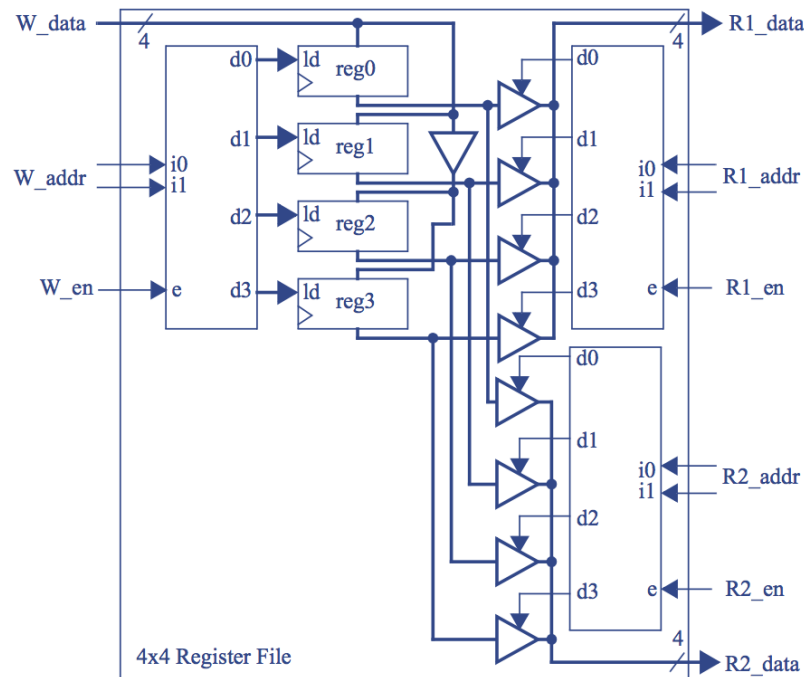4.62 Solution: (10', should be all correct, careless mistakes -2')



4.64 Solution: (10', should be all correct, careless mistakes -2')

a) $W_data = 1110$, $W_addr = 11$, $W_en = 1$, $R_addr = 11$, $R_en = 1$

b) Before rising edge:

$R0 = 0101$

$R1 = 0101$

$R2 = 0101$

$R3 = 0101$

$R_data = 0101$

After rising edge:

$R0 = 0101$

$R1 = 0101$

$R2 = 0101$

$R3 = 1110$

$R_data = 1110$