

# Homework 2

Huy Quang Lai  
132000359

*Texas A&M University*

29 September 2022

An Aggie does not lie, cheat or steal.  
Nor does an Aggie tolerate those who do.

---

## Chapter 4

### 4.2

 


Figure 1: Timing Diagram

## 4.3

 


Figure 2: 4-bit Register

## 4.10

The maximum time delay for both the full adder and the half adder is 3 ns. Therefore, eight adders will have a total delay of 24 ns. However, the carry out of a half-adder will be correct after 2ns instead of 3ns. Since a half adder can be used to add the least significant bit of the numbers, the 8-bit sum will be correct by 23 ns.

## 4.13

 


Figure 3: Quad 8-bit adder

 
**4.21**

Figure 4: 16-bit Magnitude Comparator

**4.30**

- (a)  $11100000_2 = 32_{10}$
- (b)  $01111111_2 = 127_{10}$
- (c)  $11110000_2 = -16_{10}$
- (d)  $11000000_2 = -64_{10}$
- (e)  $11100000_2 = -32_{10}$

**4.33**

- (a)  $29_{10} = 00011101_2$
- (b)  $100_{10} = 01100100_2$
- (c)  $125_{10} = 01111101_2$
- (d)  $-29_{10} = 11100011_2$
- (e)  $-100_{10} = 10011100_2$
- (f)  $-125_{10} = 10000011_2$
- (g)  $-2_{10} = 11111110_2$

## 4.40

 



Figure 5: Arithmetic Logic Unit

Operation of the AL-Extender is as follows.

$x$	$y$	$z$	S	$a_o$	$b_o$	$c_o$
0	0	0	$A - B$	$a$	$b'$	1
0	0	1	$A + B$	$a$	$b$	0
0	1	0	$A * 8$	$a \ll 3$	0	0
0	1	1	$A / 8$	$a \gg 3$	0	0
1	0	0	$A \text{ NAND } B$	$a \text{ NAND } b$	0	0
1	0	1	$A \text{ XOR } B$	$a \text{ XOR } b$	0	0
1	1	0	Reverse $A$	$a$ reversed	0	0
1	1	1	NOT $A$	NOT $a$	0	0

Table 1: AL Extender Functionality

## 4.62

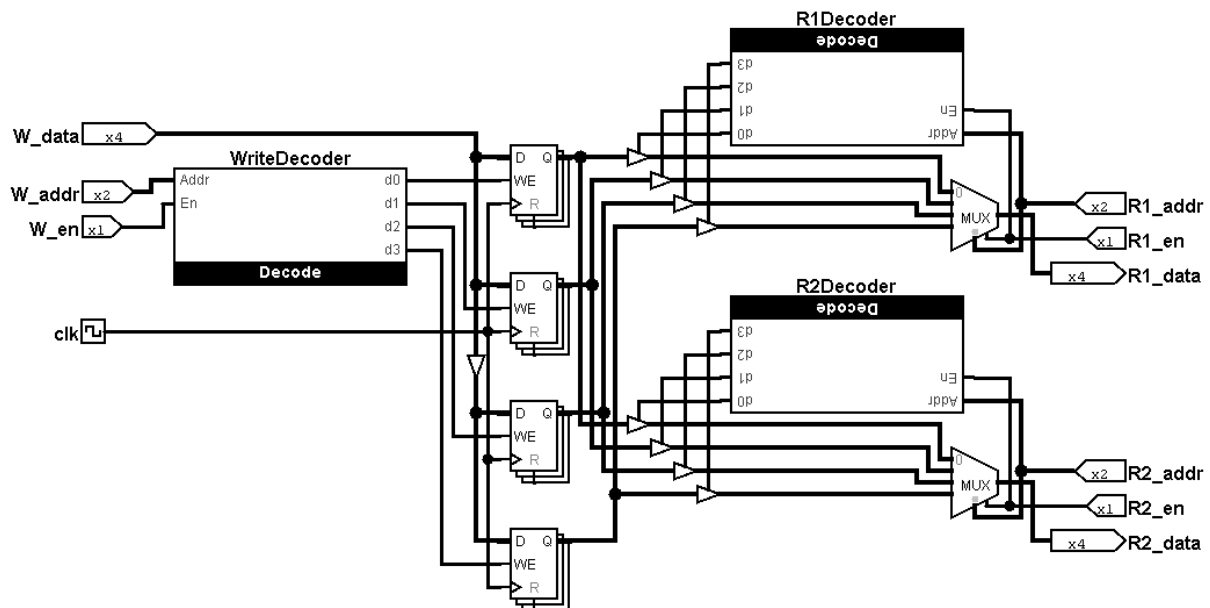Figure 6:  $4 \times 4$  Register File

## 4.64

(a)  $W_{data} = 1110, W_{addr} = 11, W_{en} = 1, R_{addr} = 11, R_{en} = 1$

(b) Before rising edge.

$$R_0 = 0101$$

$$R_1 = 0101$$

$$R_2 = 0101$$

$$R_3 = 0101$$

$$R_{data} = 0101$$

After rising edge.

$$R_0 = 0101$$

$$R_1 = 0101$$

$$R_2 = 0101$$

$$R_3 = 1110$$

$$R_{data} = 1110$$