

# Lab 2 Report



Huy Quang Lai  
132000359

*Texas A&M University*

15 September 2022

---

An Aggie does not lie, cheat or steal.  
Nor does an Aggie tolerate those who do.

  **Problem 1**Figure 1:  $F = abc + ab + a + b + c$ Figure 2:  $G = a'b'c + ab'c + abc$

Chips used: 74LS04 inverter gate, 74LS08 quad 2-input AND gate, and 74LS32 quad 2-input OR gate.

To physically wire circuit  $F$

Parameters:

$$V_{cc} = 5V, T_A = 25^\circ C, C_L = 15pF, R_L = 2k\Omega$$

Maximum delay, for  $F$  would be  $2t_{OR} + 2t_{AND}$ . This is equivalent to  $2(11) + 2(13) = 48ns$ . Likewise for  $G$ , its time delay would be  $t_{NOT} + 2t_{AND} + 2t_{OR}$ . This is equivalent to  $10 + 2(13) + 2(11) = 58ns$ .

The maximum delay under the indicated parameters would be 48 nanoseconds for Circuit  $F$  and 58 nanoseconds for Circuit  $G$ .

## Problem 2